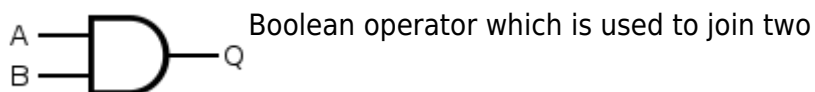


Logic Gates

Overview


This page gives a brief description of the principal logic gates, a detailed description will be found in Wikipedia by clicking on each of the images. A more detailed overview is in [Wikipedia here](#).

AND




statements so that the final statement is true only if the individual statements are all true. Thus $(X > 1) \text{AND} (X < 2)$ is true if X is between 1 and 2.

OR

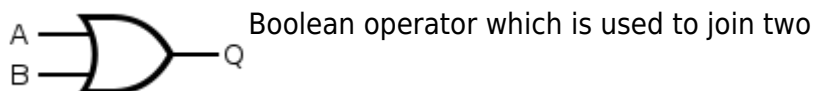


statements so that the final statement is true if either of the individual statements are true.

NAND

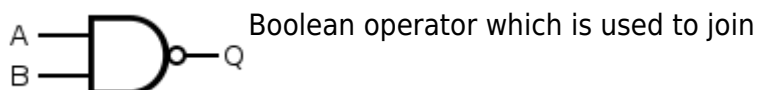

two statements so that the final statement is false only if the individual statements are all true. Inverted AND.

NOR

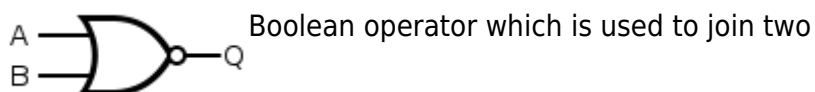

statements so that the final statement is false if either of the individual statements are true. Inverted OR.

XOR



Exclusive OR. Boolean operator which is used to join two

statements so that the final statement is true if one or other of the individual statements are true but not both.

From:

https://www.merg.org.uk/merg_wiki/ - Knowledgebase

Permanent link:

https://www.merg.org.uk/merg_wiki/doku.php?id=glossary:logicgates&rev=1366089351

Last update: **2014/11/11 13:28**

